



WORKBENCH

ideas

QST Reviews

Electain KPA1500 Legal-Limit HF and 6-Meter Linear Amplifier

Harger Uni-Shot Exothermic Ground Connection Welding Kits

W40P Magnetic Loop Antenna with Remote Tuning

MFJ-1708SDR and MFJ-1708B-SDR TR Switches

Pacific Antenna Low-Pass Filter Kit

DIGITAL FEATURE



49 | See our Video of the Elecraft KPA1500 Legal-Limit HF and 6-Meter Linear Amplifier.



Howard E. Michel, WB2ITX

Steve Ford, WB8IMY Editor

Becky R. Schoenfeld, W1BXY Managing Editor

Jen Glifort, KC1KNL Caroline Kenney Allison McLellan Assistant Editors

Bart Jahnke, W9JJ Contest Branch Manager

Rick Lindquist, WW1ME Happenings

Bob Allison, WB1GCM Product Review Lab Testing

Mark J. Wilson, K1RO
AI Brogdon, W1AB
Bernie McClenny, W3UR
H. Ward Silver, N0AX
Paul Wade, W1GHZ
Jon Jones, N0JK
Rick Palm, K1CE
Joel R. Hallas, W1ZR
Barry Shackleford, W6YE
Kai Siwiak, KE4PT
Bruce Draper, AA5B
Contributing Editors

Michelle Bloom, WB1ENT Production Supervisor

Jodi Morin, KA1JPA Assistant Production Supervisor

Maty Weinberg, KB1EIB Production Coordinator

Sue Fagan, KB10KW Graphic Design Supervisor

David Pingree, N1NAS Senior Technical Illustrator

Janet Rocco, W1JLR Advertising Sales Manager

Bob Inderbitzen, NQ1R Marketing Manager


Yvette Vinci, KC1AIM Circulation Manager

Diane Szlachetka, KB10KV Advertising Graphics Designer

Steve Ewald, WV1X
Field Organization Supervisor

Eric CaseyConvention and Event Coordinator

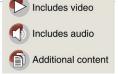Contents March 2019 • Volume 103 • Number 3



9 Second Century
Toward a More Secure Future

An Arduino-Powered RF Detector Teri Bloom, AC5YL

A Portable End-Fed Half-Wave Antenna for 80 Meters Rick Littlefield, K1BQT

Build a 9 to 1 Unun Transformer Stan Johnson, W0SJ

36 Improve Workbench Safety with GFCI and a Kill Switch Allen Wolff, KC70

37 3D-Printed Coax-to-Wire Connection Blocks John Portune, W6NBC

39 Super Simple 6-Meter SDR Transceiver James Forkin, WA3TFS

Soldering Surface-Mount Devices
Dino Papas, KL0S

Product Review
Mark Wilson, K1RO

Elecraft KPA1500 Legal-Limit HF and 6-Meter Linear Amplifier; Harger Uni-Shot Exothermic Ground Connection Welding Kits; W4OP Magnetic Loop Antenna with Remote Tuning; MFJ-1708SDR and MFJ-1708B-SDR TR Switches; Pacific Antenna Low-Pass Filter Kit



Youth at Sea Activate Market Reef — OJOC Pieter Ketsman, ON3DI, and Horia Ilie, YO3IMD

Canadian National Parks on the Air 2019
Sean Kutzko, KX9X

70 ARRL's New Podcast for New Hams

71 Lithuanian Radiosport Henryk Kotowski, SM0JHF

74 Judging Regional Science and Engineering Fairs Bill Vining, N5YZ

77 Choosing Gear for Portable Activations T.J. "Skip" Arey, N2EI

Nominations Now Being Accepted for 2019 McGan Silver Antenna Award for Excellence in Public Relations

ARRL International Grid Chase Update

The 2018 IARU HF World Championship Results
Bob Raymond, WA1Z

72 The April 2019 ARRL Rookie Roundup — Phone

Columns

Classic Radio	86
Contest Corral	88
Correspondence	24
The Doctor is In	58
Eclectic Technology	64
Happenings	81
Hints & Hacks	62
How's DX?	94
Member Spotlight	13
Public Service	84
Technical Correspondence	60
Up Front	20
The World Above 50 MHz	96
75/50/25 Years Ago	102

Digital and Mobile Editions

ARRL members can access the digital edition via a link at **www.arrl.org/qst**, download our iOS app from the iTunes Store, and download our Android app from the Google Play Store.

Departments

Amateur Radio Band Chart	101
ARRL Member Benefits	14
ARRL Section Managers	16
ARRL VEC Honor Roll	98
Convention and Hamfest Calendar.	99
Feedback	79
Field Organization Reports	102
Ham Ads	140
Index of Advertisers1	42, 143
New Products	38, 79
Officers, Division Directors, and Sta	aff 15
QuickStats	130
Silent Keys	103
Special Event Stations	98
W1AW Qualifying Runs	100
W1AW Schedule	93

Interested in Writing for QST?

www.arrl.org/qst-author-guide email: qst@arrl.org



Our Cover

This month, *QST* offers a wealth of workbench projects and ideas that involve everything from basics like soldering and electrical safety to leading technologies like SDR and 3D printing. Whether your approach to ham radio is old-school or cutting edge, this issue has something you can use.













QST (ISSN:0033-4812) is published monthly as its official journal by the American Radio Relay League, Inc, 225 Main St., Newington, CT 06111-1400, USA. Periodicals postage paid at Hartford, CT, USA and at additional mailing offices.

POSTMASTER: Send address changes to: QST, 225 Main St., Newington, CT 06111-1400, USA. Canada Post: Publications Mail Agreement #90-0901437. Canada returns to be sent to IMEX Global Solutions, 1501 Morse Ave., Elk Grove Village, IL 60007.

US & Possessions: Membership in the ARRL, including a 1-year subscription to QST, is available to individuals at \$49. Licensed radio amateurs age 21 and under and the eldest licensee in the household may qualify for the rate of \$25. Life Membership, including a subscription to QST is available at \$1,225.* Membership includes \$21 per year for subscription to QST. Membership and QST cannot be separated. Libraries and institutions, \$49 per year. Single copies \$6.95.

International

To compensate for additional postage for mailing outside the US, the following rates apply:

Canada: Membership in the ARRL, including a 1-year subscription to QST, \$62, payable in US funds. Life Membership, including a subscription to QST is available at \$1,550.* Libraries and institutions, \$62 per year.

All Other Countries: Membership in the ARRL, including a 1-year subscription to *QST*, \$76, payable in US funds. Life Membership, including a subscription to *QST*, is available at \$1,900.* Libraries and institutions, \$76 per year.

Membership without *QST* is available to the immediate family of a member living at the same address, and to anyone who is legally blind, for \$10 per year.

Foreign remittances should be by international postal or express money order or bank draft negotiable in the US and for an equivalent amount in US funds. Membership in the ARRL, including a 1-year subscription to Digital *QST* only, is available to Canadian and International members at \$49

Copyright © 2019 by the American Radio Relay League Inc. Title registered at the US Patent Office. International copyright secured. All rights reserved. Quedan reservados todos los derechos. Printed in the USA.

OST®, DXCC®, VUCC®, DX Century Club®, ARES®, Amateur Radio Emergency Service®, Logbook of The World®, LoTW®, and ARRL, the national association for Amateur Radio® are registered trademarks of the American Radio Relay League, Inc.

The ARRL and *QST* in no way warrant the products described or reviewed herein.

QST is available to blind and physically handicapped individuals from the Library of Congress, National Library Service for the Blind and Physically Handicapped. Call 1-800-424-8567 or go to www.loc.gov/nls/.

Indexed by Applied Science and Technology Index, Library of Congress Catalog Card No: 21-9421.

*Payment arrangements available. Please write for details.

In order to ensure prompt delivery, we ask that you periodically check the address information on your mailing label. If you find any inaccuracies, please contact the Circulation Department at circulation@arrl.org or 860-594-0200 immediately. Thank you for your assistance.

Reprints and permissions: permission@arrl.org Details of our Online Privacy Policy can be found at www.arrl.org/online-privacy-policy.

Telephone: **860-594-0200** Fax: **860-594-0259**



Build a 9 to 1 **Unun Transformer**

to-unbalanced transformer can be built with easy-to-find parts.

Step by Step

Stan Johnson, WOSJ

An end-fed long wire antenna is typically fed with a 9 to 1 impedance ratio unun. I used a Laird 28B1540-000 core (Digi-Key part number 240-2319-ND). It has a 1.54-inch outer diameter and a 0.66-inch inner diameter, is 0.875-inch long, and costs less than a couple of dollars.

My unun is wound with #16 AWG Teflon™ insulated wire. I used three

different colors to keep the wires organized and make the connections foolproof while white shrink tubing from a Harbor Freight Tools assortment package holds the wires together.

pieces — two are 17 inches long and one is 20 inches. I used three

For additional detailed instructions with photos, please see the QST in Depth web page at www.arrl.org/qst-in-depth. Step 1: Slip a ½-inch piece of shrink tubing over the three wires and

position them up through the center of the core with the tubing centered on the outside. I placed the black wire on the left, white in the center, and longer blue on the right. Leave 2½ inches of wire sticking above the center of the core.

Step 2: Wrap a second turn and add another piece of shrink tubing. Make sure that the wires have not become twisted in the center of the core.

Step 3: Wind another two turns, adding shrink tubing and making sure the wires do not become twisted in the center of the core. Insert a piece of ½-inch plastic tubing in the center to hold the windings. Space all the windings at 90° to each other.

Step 4: The long end of the 20-inch blue wire goes to the antenna. The short end of the blue wire connects to the white wire that protrudes from the opposite end of the core. Trim and solder so that the wires remain snug against the core.

Step 5: Trim about ½ inch of insulation from the remaining end of the white wire. Cut the white insulation at the corner of the core and slide it about 1/4 inch towards the wire end. Cut and trim the black wire from the bottom of the core, wrapping it around the white wire close to the core, and solder the connection.

Step 6: Add shrink tubing over the soldered connections. Install a zip tie around the unun to keep the windings pressed against the core.

The unun acts as a transformer with a 3 to 1 turns ratio (9 to 1 impedance ratio) as long as the windings are phased correctly. The dots in Figure 1 indicate the phasing of the windings.

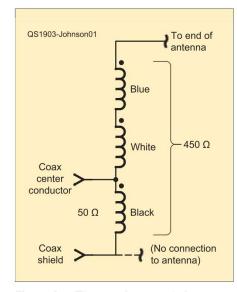


Figure 1 — The unun is connected according to this diagram.


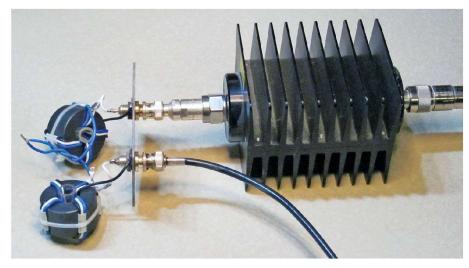


Figure 2 — A test configuration using two identical ununs positioned back to back.

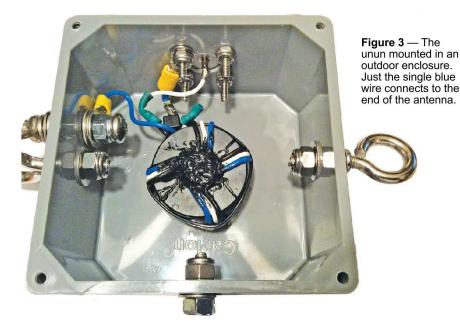

Testing

Solder the shield side of a coax connector to the black wire and the center conductor to the white wire. Connect a signal generator to the coax connector. Connect the first oscilloscope probe to the white wire and the second scope probe to the free end of the blue wire. Attach the probe ground clips to the PC board, as shown in Picture J on the *QST* in Depth page. You should see a voltage on the blue wire that is in-phase and three times the voltage on the white wire.

In another test, connect the unun to a 450 Ω resistor from the blue wire to the black wire (the shield connection). Measure the input impedance with an antenna analyzer. You should read around 50 Ω .

I tested the ununs at 100 W by connecting two ununs back to back in series. The first unun transforms the impedance to 450 Ω and the second transformed it back down to 50 Ω . Because the ununs are identical, I divided the measured power loss in decibels by two.

Table 1 Insertion loss per unun		
Band (meters)	Loss (dB)	
160	0.32	
80	0.20	
40	0.15	
20	0.18	
15	0.21	
10	0.26	

I connected the transmitter through a barrel connector to a 50 dB, 100 W attenuator and measured the RF power with a Hewlett-Packard 436A power meter, using an 8482A power sensor to get a reference power level in dBm. I then replaced the barrel connector with the two ununs (see Figure 2). The last step is to key the transmitter and record the dBm reading divided by two. Table 1 lists the unun measured losses across the MF-HF bands.

Figure 3 shows the finished unun in an outdoor enclosure.

All photos by the author.

Stan Johnson, WOSJ, was first licensed in 1961, and upgraded to Amateur Extra class in 1968. He has a degree in electronics from Iowa State University and a physics degree from the University of Northern Iowa. His career began at Bell Telephone Laboratories near Chicago and ended at the John Deere Product Engineering Center in Iowa as Scientist/Engineer. Since retiring in 2001, Stan enjoys building things, mostly out of junk. You can reach Stan at w0scavengesjunk@gmail.com.

For updates to this article, see the QST Feedback page at www.arrl.org/feedback.



